

Fig. 1.23.

The current  $I$  will flow through 7 ohms resistor also. The power absorbed by it will be

$$(6^2) (7) = 252 \text{ W (Ans).}$$

Referring to Fig. 23-B and applying the current division technique of equation (1.29).

$$I_2 = \frac{I(R_1)}{R_1 + R_2} = \frac{6 \times 4}{4 + 12} = 1.5 \text{ A}$$

Current in 7 ohm resistor = current in 5 Ω resistor =  $I_2$ , as they are in series

$$\therefore \text{Power absorbed by } 7 \Omega \text{ resistor} = (1.5^2) 7 = 15.75 \text{ W (Ans).}$$

$$\text{Power absorbed by } 5 \Omega \text{ resistor} = (1.5)^2 \times 5 = 11.25 \text{ W (Ans).}$$

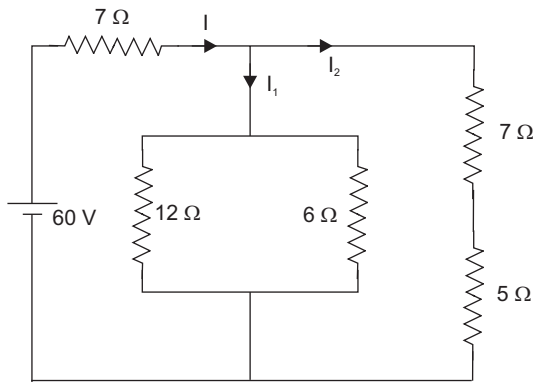


Fig. 1.23A.

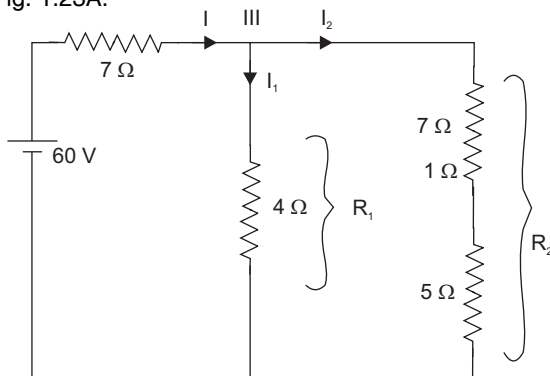


Fig. 1.23B. Circuit for illustration 18 with current directions marked, for evaluation of  $I_2$

The current  $I$  hence is,  $60/10 = 6 \text{ A}$

The power delivered by the source is the product of its  $V$  and  $I$ . That is  $60 \times 6 = 360 \text{ W (Ans).}$

### Illustration 19

Three resistors of 2, 5 and 10 Ω are joined in parallel and a total current of 24 A is passed through them. Find the current through each resistor.

### Solution

The problem is depicted in Fig. 1.24.

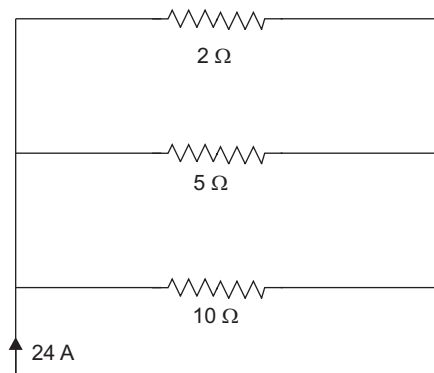


Fig. 1.24. Circuit for illustration 19